

Weifan Lin  
Csc343  
05/14/2015

## Keyboard

### Objectives:


The goal of this lab was to gain an understanding of the ps2 communication protocol and to design and implement a ps2 keyboard. At the end of this lab, we wished to be able to print out our name based on input from a ps2 keyboard.

### Specifications:

- PS2 Receiver – This system has five 1-bit input signals, Clk, Reset, ps2Data, ps2Clock, and rec\_en. Also, this system has two output signals, a 1-bit rec\_done signal, and a 8-bit Dout signal.
- Shift Dectector – This system has three input signal, two 1-bit signals, clk and done, and one 8-bit signal, scan. Also, this system has one 1-bit output signal, shift.
- Ascii Converter – This system has two input signals, a 1-bit shift signal and an 8-bit scan\_code signal. Also, this system has an 8-bit output signal, ascii.
- Keyboard Interface – This system has three 1-bit input signals, Clock, Reset, and En, and three output signals, two 1-bit signals, ps2D and ps2C, and one 56-bit display signal. This system requires the ps2 receiver, the shift detector, and the ascii converter.
 
## Functionality:

- PS2 Receiver – This system has two functions, one of which is to output the scan codes of the keys on the keyboard being pressed, and the other being to correctly identify the scan codes and neglect noise or jitter. To perform the first function, the ps2 receiver uses a finite state machine with three states, idle, receive, and done. This finite state machine is shown below in Figure 1, where the variable N represents a count down of the iterations of the system.



- Shift Detector – The function of the shift detector is to determine when the “Shift” button on the keyboard has been pressed. To accomplish this task, a finite state machine with three states, idle, pressed, and released, is used. This finite state machine is illustrated below in Figure 3, where scan represents the scan codes captured from the previous system, PS2 Receiver.
- Keyboard Interface – The function of this system is to map together all the previous components to a seven-segment display system that will display not only the ASCII conversion of the keys, but also the scan codes. To display the ASCII and scan codes on the seven-segment display, this system utilizes another system, the Hex to Seven converter. The Hex to Seven converter's function is to map


together eight seven- segment displays to display a thirty-two bit input signal.

## Design:

Scan Code to Ascii:

```
1  LIBRARY IEEE;
2  USE IEEE.STD_LOGIC_1164.all;
3  USE IEEE.STD_LOGIC_ARITH.all;
4  USE IEEE.STD_LOGIC_UNSIGNED.all;
5
6  entity scan_code_to_ascii is
7  port(
8      scan_code: in std_logic_vector(7 downto 0);
9      shift: in std_logic;
10     ascii: out std_logic_vector(7 downto 0)
11 );
12 end scan_code_to_ascii;
13
14 architecture arch of scan_code_to_ascii is
15
16 begin
17
18     ascii <= "01010111" when shift='1' and scan_code="00011101" --1D W
19             else "01100101" when shift='0' and scan_code="00100100" --24 e
20             else "01101001" when shift='0' and scan_code="01000011" --43 i
21             else "01000110" when shift='1' and scan_code="00101011" --2B F
22             else "01100001" when shift='0' and scan_code="01000011" --1C a
23             else "01101110" when shift='0' and scan_code="00011100" --31 n
24
25 end arch;
```

Keyboard:

 

## Testing on DE2 Board

 


Figure above represents letter i

 


Figure above represents letter n

 


Figure above represents letter a

### **Conclusion:**

The objective of this lab was achieved because after designing the individual part that make up the keyboard interface, we tested the system on the DE2 board and it preformed as expected. The first system we had to make was the PS2 Receiver, which interprets the keys the user pressed into scan codes. The next system was the shift detector, which takes the scan code from the previous system and determines if the shift key was pressed. The final system combines the two previous systems and converts the scan code and shift signal into the ascii representation of the key being pressed.

```

1  LIBRARY IEEE;
2  USE IEEE.STD_LOGIC_1164.all;
3  USE IEEE.STD_LOGIC_ARITH.all;
4  USE IEEE.STD_LOGIC_UNSIGNED.all;
5
6  entity scan_code_to_ascii is
7  port(
8      scan_code: in std_logic_vector(7 downto 0);
9      shift: in std_logic;
10     ascii: out std_logic_vector(7 downto 0)
11 );
12 end scan_code_to_ascii;
13
14 architecture arch of scan_code_to_ascii is
15
16 begin
17
18     ascii <= "01010111" when shift='1' and scan_code="00011101" --1D W
19             else "01100101" when shift='0' and scan_code="00100100" --24 e
20             else "01101001" when shift='0' and scan_code="01000011" --43 i
21             else "01000110" when shift='1' and scan_code="00101011" --2B F
22             else "01100001" when shift='0' and scan_code="01000011" --1C a
23             else "01101110" when shift='0' and scan_code="00011100" --31 n|
24
25 end arch;

```

## Appendix:

Pin assignments:

To, Location

Reset, PIN\_G26

Clock, PIN\_N2

En, PIN\_N23

ps2D, PIN\_C24

ps2C, PIN\_D26

display[0], PIN\_AF10

display[1], PIN\_AB12

display[2], PIN\_AC12

display[3], PIN\_AD11

display[4], PIN\_AE11  
display[5], PIN\_V14  
display[6], PIN\_V13  
display[7], PIN\_V20  
display[8], PIN\_V21  
display[9], PIN\_W21  
display[10], PIN\_Y22  
display[11], PIN\_AA24  
display[12], PIN\_AA23  
display[13], PIN\_AB24  
display[14], PIN\_AB23  
display[15], PIN\_V22  
display[16], PIN\_AC25  
display[17], PIN\_AC26  
display[18], PIN\_AB26  
display[19], PIN\_AB25  
display[20], PIN\_Y24  
display[21], PIN\_Y23  
display[22], PIN\_AA25  
display[23], PIN\_AA26  
display[24], PIN\_Y26  
display[25], PIN\_Y25  
display[26], PIN\_U22  
display[27], PIN\_W24  
display[28], PIN\_U9

display[29], PIN\_U1  
display[30], PIN\_U2  
display[31], PIN\_T4  
display[32], PIN\_R7  
display[33], PIN\_R6  
display[34], PIN\_T3  
display[35], PIN\_T2  
display[36], PIN\_P6  
display[37], PIN\_P7  
display[38], PIN\_T9  
display[39], PIN\_R5  
display[40], PIN\_R4  
display[41], PIN\_R3  
display[42], PIN\_R2  
display[43], PIN\_P4  
display[44], PIN\_P3  
display[45], PIN\_M2  
display[46], PIN\_M3  
display[47], PIN\_M5  
display[48], PIN\_M4  
display[49], PIN\_L3  
display[50], PIN\_L2  
display[51], PIN\_L9  
display[52], PIN\_L6  
display[53], PIN\_L7



display[54], PIN\_P9

display[55], PIN\_N9

Keyboard interface VHDL:

LIBRARY ieee;

USE ieee.std\_logic\_1164.all;

ENTITY keyboard\_interface IS

PORT

(

Clock : IN STD\_LOGIC;

Reset : IN STD\_LOGIC;

En : IN STD\_LOGIC;

display: out std\_logic\_vector(55 downto 0);

ps2D : INOUT STD\_LOGIC;

ps2C : INOUT STD\_LOGIC

);

END keyboard\_interface;

ARCHITECTURE bdf\_type OF keyboard\_interface IS

COMPONENT ps2\_rec

PORT(Clk : IN STD\_LOGIC;

Reset : IN STD\_LOGIC;

ps2Data : IN STD\_LOGIC;

```

        ps2Clock : IN STD_LOGIC;

        rec_en : IN STD_LOGIC;

        rec_done : OUT STD_LOGIC;

        Dout : OUT STD_LOGIC_VECTOR(7 DOWNTO 0)

    );

END COMPONENT;

```

```

COMPONENT hex_to_sevenPORT(en : IN STD_LOGIC;

    input : IN STD_LOGIC_VECTOR(31 DOWNTO 0);

    HEX0 : OUT STD_LOGIC_VECTOR(6 DOWNTO 0);

    HEX1 : OUT STD_LOGIC_VECTOR(6 DOWNTO 0);

    HEX2 : OUT STD_LOGIC_VECTOR(6 DOWNTO 0);

    HEX3 : OUT STD_LOGIC_VECTOR(6 DOWNTO 0);

    HEX4 : OUT STD_LOGIC_VECTOR(6 DOWNTO 0);

    HEX5 : OUT STD_LOGIC_VECTOR(6 DOWNTO 0);

    HEX6 : OUT STD_LOGIC_VECTOR(6 DOWNTO 0);

    HEX7 : OUT STD_LOGIC_VECTOR(6 DOWNTO 0)

);

END COMPONENT;

```

```

COMPONENT shift_detector

    PORT(clk : IN STD_LOGIC;

        done : IN STD_LOGIC;

        hex : IN STD_LOGIC_VECTOR(7 DOWNTO 0);

        shift : OUT STD_LOGIC

```

```

    );
END COMPONENT;

COMPONENT scan_code_to_ascii
    PORT(shift : IN STD_LOGIC;
          scan_code : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
          ascii : OUT STD_LOGIC_VECTOR(7 DOWNTO 0)
    );
END COMPONENT;

```

```

SIGNAL    NotReset : STD_LOGIC;
SIGNAL    rec_done : STD_LOGIC;
SIGNAL    dis_input : STD_LOGIC_VECTOR(31 DOWNTO 0);
SIGNAL    ScanCode : STD_LOGIC_VECTOR(7 DOWNTO 0);
SIGNAL    shift_output : STD_LOGIC;
SIGNAL    asci_output : STD_LOGIC_VECTOR(7 DOWNTO 0);

```

```

BEGIN

```

```

rec : ps2_rec

```

```

PORT MAP(Clk => Clock,

```

```
Reset => NotReset,  
ps2Data => ps2D,  
ps2Clock => ps2C,  
rec_en => En,  
rec_done => rec_done,  
Dout => ScanCode );
```

```
sev : hex_to_seven
```

```
PORT MAP(en => rec_done,  
input => dis_input,  
HEX0 => display(6 downto 0),  
HEX1 => display(13 downto 7),  
HEX2 => display(20 downto 14),  
HEX3 => display(27 downto 21),  
HEX4 => display(34 downto 28),  
HEX5 => display(41 downto 35),  
HEX6 => display(48 downto 42),  
HEX7 => display(55 downto 49)  
);
```

```
dis_input <= asci_output & "0000000000000000" & ScanCode;
```

```
NotReset <= NOT(Reset);
```

```

shft : shift_detector

PORT MAP(clk => Clock,

          done => rec_done,

          hex => ScanCode,

          shift => shift_output);

ascii : scan_code_to_ascii

PORT MAP(shift => shift_output,

          scan_code => ScanCode,

          ascii => ascii_output);

END bdf_type;

```

## PS2 Receiver VHDL

```

library ieee;

use ieee.std_logic_1164.all;

use ieee.numeric_std.all;

entity ps2_rec is

    port

    (

        Clk ,Reset: in std_logic;

        ps2Data : in std_logic;

        ps2Clock : in std_logic;

        rec_en : in std_logic;

        rec_done: out std_logic;

        Dout: out std_logic_vector(7 downto 0)
    )

```

```
);  
end ps2_rec;
```

architecture arch of ps2\_rec is

```
type statetype is (idle, receive, done);  
signal current_state, next_state : statetype;  
signal current_data, next_data: std_logic_vector(10 downto 0);  
signal current_n, next_n      : unsigned(3 downto 0);  
signal fall_edge: std_logic;  
signal current_filter, next_filter : std_logic_vector(7 downto 0);  
signal current_filter_clock, next_filter_clock : std_logic;
```

```
begin
```

```
process(clk, reset)
```

```
begin
```

```
    if reset = '1' then
```

```
        current_filter <= (others => '0');
```

```
        current_filter_clock <= '0';
```

```
    elsif (rising_edge(clk)) then
```

```
        current_filter <= next_filter;
```

```
        current_filter_clock <= next_filter_clock;
```

```
    end if;
```

```
end process;
```

```
next_filter <= ps2clock & current_filter(7 downto 1);
next_filter_clock <= '1' when current_filter = "11111111" else
    '0' when current_filter = "00000000" else
    current_filter_clock;
fall_edge <= current_filter_clock and (not next_filter_clock);
```

```
process (Clk, reset)
begin
    if(reset = '1') then
        current_state <= idle;
        current_n <= (others => '0');
        current_data <= (others => '0');
    elsif(rising_edge(Clk)) then
        current_state <= next_state;
        current_n <= next_n;
        current_data <= next_data;
    end if;
end process;
```

```
process(current_state, current_data, current_n, ps2Data, fall_edge)
begin
    rec_done <= '0';
    next_state <= current_state;
```

```

next_n <= current_n;

next_data <= current_data;

case current_state is

    when idle =>

        if(fall_edge = '1' and rec_en = '1') then

            next_data <= ps2Data & current_data(10 downto 1);

            next_n <= "1001";

            next_state <= receive;

        end if;

    when receive =>

        if(fall_edge = '1') then

            next_data <= ps2Data & current_data(10 downto 1);

            if current_n = 0 then

                next_state <= done;

            else

                next_n <= current_n - 1;

            end if;

        end if;

    when done =>

        next_state <= idle;

        rec_done <= '1';

end case;

end process;

Dout <= current_data(8 downto 1);

```



```
end arch;
```

### Shift Detector VHDL

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
use ieee.numeric_std.all;
```

```
entity shift_detector is
```

```
    port
```

```
        (clk, done: in std_logic;
```

```
         hex: std_logic_vector(7 downto 0);
```

```
         shift: out std_logic
```

```
    );
```

```
end shift_detector;
```

```
architecture arch of shift_detector is
```

```
    type statetype is (idle, shft, f0, pause);
```

```
    signal current_state, next_state : statetype;
```

```
begin
```

```
    process(clk)
```

```
    begin
```

```
        if(rising_edge(clk)) then
```

```

        current_state <= next_state;
end if;

end process;

process(hex, done)
begin

    shift <= '0';
    next_state <= current_state;

    case current_state is
        when idle =>
            shift <= '0';

            if(done = '1' and hex = "00010010") then
                next_state <= shft;
            end if;

            when shft =>
                shift <= '1';

                if(done = '1' and hex = "11110000") then
                    next_state <= f0;
                end if;

```

```
when f0 =>
  shift <= '1';
  if(done = '1') then
    if(hex= "00010010") then
      next_state <= idle;
    else
      next_state <= shft;
    end if;
  end if;

when pause =>
  shift <= '1';

end case;

end process;

end arch;
```