

CS 343

Simplified Single Cycle CPU with ADD/SUB instructions only

in VHDL and Model-SIM , Quartus, DE 2-70

March 27, 2015

Instructor: Professor Izidor Gertner

Design components:

1. 16 bit Instruction Register to store 16 bit instruction
2. 16 bit Program Counter Register
3. 16 16 bit word Register File
4. ADD/Sub instruction DATAPATH
5. Instruction decode unit to decode 2 bit opcode to required control signals ALUctr RegWr

Optional : Instruction FETCH UNIT, BEQ instruction


Lab Assignments

Use the same techniques you have used to build SRAM in the previous lab.

Design 16 bit Instruction Register, to store the currently executing instruction.

Instruction Register

 
Stores the instruction
During the execution
time



EXTEND THE SRAM DESIGN YOU HAVE SUBMITTED on MARCH 20 to
REGISTER FILE

- Register File consists of 16 registers:

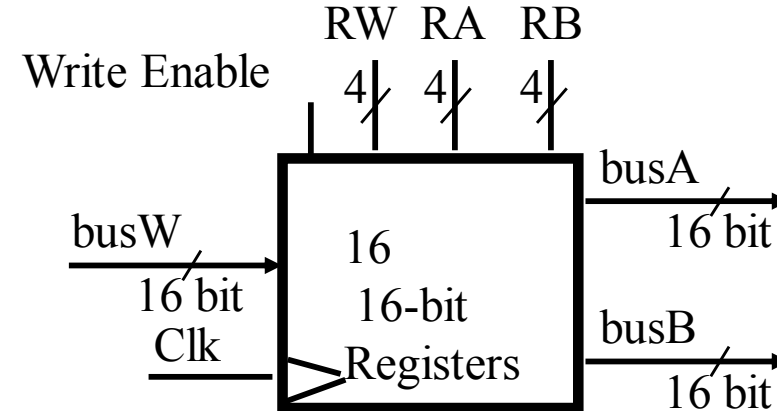- Two 16-bit output busses:
busA and busB
- One 16-bit input bus: busW



- Register is selected by:

- RA (4 bit number) selects the register to put on busA (data)
- RB (4 bit number) selects the register to put on busB (data)
- RW (4 bit number) selects the register to be written via busW (16 bit data) when Write Enable is 1

- Clock input (CLK)

- The CLK input is a factor ONLY during write operation
- ***During read operation, Register File behaves as a combinational logic block:***
 - RA or RB valid => busA or busB valid after “access time.”

Add & Subtract Instruction

Add operation opcode bit[15]=0, bit[14]=0

Sub operation opcode bit[15]=0, bit[14]=1


Control signal $ALUctr = 1$ for SUB operation

Control signal $ALUctr = 0$ for ADD operation

Control signal $RegWrr = 1$ for write register **rd** operation

Instruction Register

 Stores the instruction
During the execution
time



PC Register


Design PC Register.

Stores the instruction address
During the execution time




Optional Instruction Fetch Unit

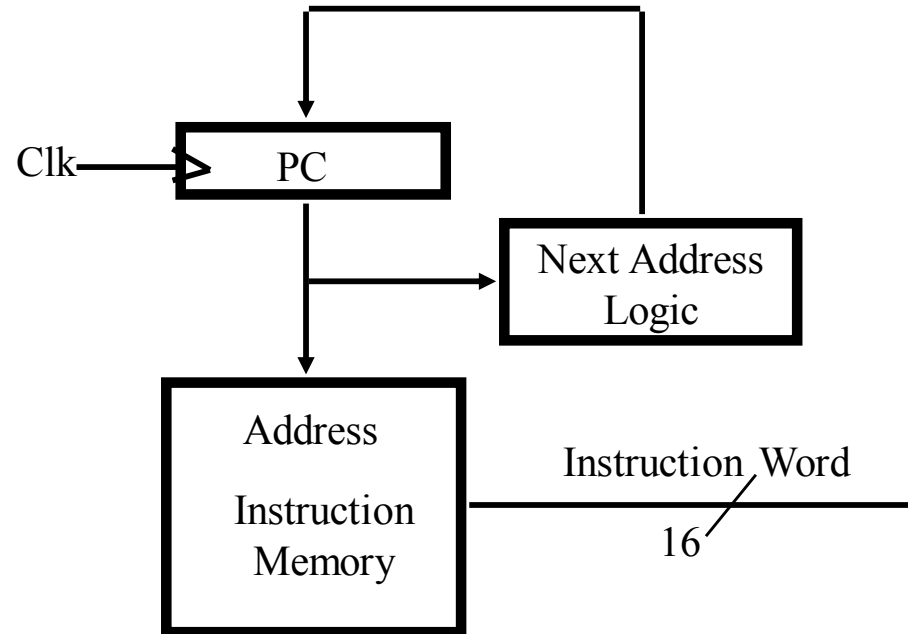- The common operations
 - Fetch the Instruction: $\text{mem}[\text{PC}]$
 - Update the program counter:
 - Sequential Code: $\text{PC} \leftarrow \text{PC} + 4$
 - Branch and Jump: $\text{PC} \leftarrow \text{"something else"}$



The Branch Instruction (optional)

 Instruction Register
Stores the instruction
During the execution
time



- `beq rs, rt, imm6`
 - `mem[PC]` Fetch the instruction from memory
 - `Equal <= (R[rs] == R[rt])` Calculate the branch condition
 - `if (Equal)` Calculate the next instruction's address
 - `PC <= PC + 4 + { SignExt(imm6) , 2b00 }`
 - `else`
 - `PC <= PC + 4`

Datapath for Branch Operations (optional)

- `beq rs, rt, imm16`

Datapath generates condition (equal)

Instruction Register
Stores the instruction
During the execution
time

