

Weifan Lin

CSc343

Lab 1

02/19/2015

## Adders

### **Objective:**

The goal of this lab was to design and understand the functioning of adders. We wanted to first build a full bit adder and use it to build a two-bit adder, and lastly build a 16-bit adder using the two-bit adder with overflow detection.

### **Specifications:**

#### Full adder inputs:

A: the first operand of the adder.

B: the second operand of the adder.

Cin (carry in): the bit that is carried in from the next less significant stage.

#### Full adder outputs:

Cout (carry out): the bit that is carried over from an addition when necessary.

S: the sum, which is last bit of the result from the addition.

Cout and S together is a 2-bit sum of the 3 inputs.

#### 2-bit adder inputs:

$A[1\dots0]$ : the first operand of the adder which is made up of four bits:  $A[1]$ , and  $A[0]$ .

$B[1\dots0]$ : the second operand of the adder which is made up of four bits:  $B[1]$ , and  $B[0]$ .

$C_{in}$ : the bit that is carried in from the less significant stage.

#### 2-bit adder outputs:

Carry: the carry output is the bit that is carried over from an addition.

$S[3\dots0]$ : The sum of the two operands which is made up of the four bits  $S[1]$ , and  $S[0]$ .

#### 16-bit adder inputs:

$A[15\dots0]$ : the first operand of the adder which is made up of four bits:  $A[15]$ ,  $A[14]$ ,  $A[13]$ , ... and  $A[0]$ .

$B[15\dots0]$ : the second operand of the adder which is made up of four bits:  $B[15]$ ,  $B[14]$ ,  $B[13]$ , ... and  $B[0]$ .

$C_{in}$ : the bit that is carried in from the less significant stage.

#### 16-bit adder outputs:

Carry: the carry output is the bit that is carried over from an addition.

$S[15\dots0]$ : The sum of the two operands which is made up of the four bits  $S[15]$ ,  $S[14]$ ,  $S[13]$ , and  $S[0]$ .

Overflow: to determine whether or not there is an overflow.

## Functionality:

### Full Adder

#### Truth Table

Inputs			Outputs	
A	B	C <sub>in</sub>	C <sub>out</sub>	S
0	0	0	0	0
1	0	0	0	1
0	1	0	0	1
1	1	0	1	0
0	0	1	0	1
1	0	1	1	0
0	1	1	1	0
1	1	1	1	1

Full adder circuit adds binary numbers and it can both carry in and carry out values. A 1-bit full adder can add three 1-bit numbers (A, B, and Cin) and produce a 2-bit output, which is made up of Cout and S.

### 2-bit Adder

A 2-bit adder is made up of 2 1-bit full adders and it adds 2 4-bit numbers, results in a 2-bit sum and when the result required a 3<sup>rd</sup> bit to carry the output, Cout yells 1, however, carry output is separated from the final sum.

## 16-bit Adder

A 16-bit adder is made up of 8 2-bit full adders and it adds 2 16-bit numbers, results in a 16-bit sum and when the result required a 17<sup>th</sup> bit to carry the output, Cout yells 1, however, carry output is separated from the final sum. This adder has an additional output to determine if there was an overflow.

### **Design:**

#### Full Adder

---

```
1  -- 1-bit Adder
2
3  LIBRARY IEEE;
4  use IEEE.STD_LOGIC_1164.ALL;
5
6  entity BIT_ADDER is
7      port( a, b, cin      : in  STD_LOGIC;
8            sum, cout      : out STD_LOGIC );
9  end BIT_ADDER;
10
11  architecture BHV of BIT_ADDER is
12  begin
13
14      sum <= (not a and not b and cin) or
15             (not a and b and not cin) or
16             (a and not b and not cin) or
17             (a and b and cin);
18
19      cout <= (not a and b and cin) or
20              (a and not b and cin) or
21              (a and b and not cin) or
22              (a and b and cin);
23  end BHV;
```

---

## 2-bit Adder

```
1  LIBRARY IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity add16 is
5      port( a, b : in STD_LOGIC_VECTOR(15 downto 0);
6            cin : in STD_LOGIC;
7            ans : out STD_LOGIC_VECTOR(15 downto 0);
8            overflow : out STD_LOGIC;
9            cout : out STD_LOGIC );
10 end add16;
11
12 architecture arch of add16 is
13
14     component add2
15         port( a, b : in STD_LOGIC_VECTOR(1 downto 0);
16               cin : in STD_LOGIC;
17               ans : out STD_LOGIC_VECTOR(1 downto 0);
18               cout : out STD_LOGIC );
19     end component;
20
21     signal c1,c2,c3,c4,c5,c6,c7,c8 : STD_LOGIC;
22     signal mux : STD_LOGIC_VECTOR(15 downto 0);
23 begin
24
25     mux(0) <= cin xor b(0);
26     mux(1) <= cin xor b(1);
27     mux(2) <= cin xor b(2);
28     mux(3) <= cin xor b(3);
29     mux(4) <= cin xor b(4);
30     mux(5) <= cin xor b(5);
31     mux(6) <= cin xor b(6);
32     mux(7) <= cin xor b(7);
```

## 16-bit Adder

```
1  LIBRARY IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity add2 is
5      port( a, b : in STD_LOGIC_VECTOR(1 downto 0);
6            cin : in STD_LOGIC;
7            ans : out STD_LOGIC_VECTOR(1 downto 0);
8            cout : out STD_LOGIC );
9  end add2;
10
11  architecture STRUCTURE of add2 is
12  component BIT_ADDER
13      port( a, b, cin : in STD_LOGIC;
14            sum, cout : out STD_LOGIC );
15  end component;
16
17  signal c1 : STD_LOGIC;
18  begin
19  b_adder0: BIT_ADDER port map (a(0), b(0), cin, ans(0), c1);
20  b_adder1: BIT_ADDER port map (a(1), b(1), c1, ans(1), cout);
21
22  END STRUCTURE;
23
24
25
26
27
28
29
30
31
32
33  mux(8) <= cin xor b(8);
34  mux(9) <= cin xor b(9);
35  mux(10) <= cin xor b(10);
36  mux(11) <= cin xor b(11);
37  mux(12) <= cin xor b(12);
38  mux(13) <= cin xor b(13);
39  mux(14) <= cin xor b(14);
40  mux(15) <= cin xor b(15);
41  b_adder0: add2 port map (a(1 downto 0), mux(1 downto 0), cin, ans(1 downto 0), c1);
42  b_adder1: add2 port map (a(3 downto 2), mux(3 downto 2), c1, ans(3 downto 2), c2);
43  b_adder2: add2 port map (a(5 downto 4), mux(5 downto 4), c2, ans(5 downto 4), c3);
44  b_adder3: add2 port map (a(7 downto 6), mux(7 downto 6), c3, ans(7 downto 6), c4);
45  b_adder4: add2 port map (a(9 downto 8), mux(9 downto 8), c4, ans(9 downto 8), c5);
46  b_adder5: add2 port map (a(11 downto 10), mux(11 downto 10), c5, ans(11 downto 10), c6);
47  b_adder6: add2 port map (a(13 downto 12), mux(13 downto 12), c6, ans(13 downto 12), c7);
48  b_adder7: add2 port map (a(15 downto 14), mux(15 downto 14), c7, ans(15 downto 14), c8);
49
50  cout <= c8;
51  overflow <= c8 xor c7;
52
53  END arch;
```

## Simulation:

### Full Adder Waveform



We have:

Case 1:  $a=0, b=0, cin=0, sum=0$  and  $cout=0$ ;

Case 2:  $a=0, b=0, cin=1, sum=1$  and  $cout=0$ ;

Case 3:  $a=0, b=1, cin=0, sum=1$  and  $cout=0$ ;

Case 4:  $a=0, b=1, cin=1, sum=0$  and  $cout=1$ ;

Case 5:  $a=1, b=0, cin=0, sum=1$  and  $cout=0$ ;


Case 6:  $a=1, b=0, cin=1, sum=0$  and  $cout=1$ ;

Case 7:  $a=1, b=1, cin=0, sum=0$  and  $cout=1$ ;

Case 8:  $a=1, b=1, cin=1, sum=1$  and  $cout=1$ ;

The results from the waveform were all correct.

### 2-Bit Adder Waveform

 

As we can see from the waveform, 2-bit adder has shown all correct results.

### 16-Bit Adder Waveform

Shown as binary:

Messages									
/test_add16/a	0111111	000111111111111111	)011111111111111111			)111111111111111111			)100000000000000000
/test_add16/b	0000000	000000000000000001			0000000000000101	)0000000000000001	1111111111111111	)0000000000000001	
/test_add16/cin	0								
/test_add16/ans	1000000	001000000000000000	)100000000000000000	0111111111111010	)000000000000000000	111111111111110	)0111111111111111		
/test_add16/cout	0								
/test_add16/overflow	1								

Shown as decimal:

/test_add16/a	8191	8191	32767		-1		-32768
/test_add16/b	1	1		5	1	-1	1
/test_add16/cin	0						
/test_add16/ans	8192	8192	-32768	32762	0	-2	32767
/test_add16/cout	0						
/test_add16/overflow	0						

We have:

Case 1: positive number + positive number = positive number with no overflow (8191+1=8192).

Case 2: positive number + positive number = positive number with overflow (32767+1= -32768).

Case 3: positive number - positive number = positive number with no overflow (32767-5=32762).

Case 4: negative + positive number = positive number with no overflow (-1+1=0).

Case 5: negative number + negative number = negative number with no overflow (-1+ -1= -2).

Case 6: negative number - positive number = positive number with overflow ( $-32768-1=32767$ ).

These results are all correct, and overflow had return right values.



## Conclusion:

The completion of this lab helped me practice a lot on using Model-SIM. Building 2-bit adder and 16-bit adder subtractor taught me how to use port mapping to simplify circuits by reusing structures. Overall the lab was a bit difficult because there was no TA to help until this week.

## Appendix:

-----1-bit Full Adder-----

```
LIBRARY IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity BIT_ADDER is
```

```
    port( a, b, cin    : in  STD_LOGIC;
```

```
          sum, cout    : out STD_LOGIC );
```

```
end BIT_ADDER;
```

```
architecture BHV of BIT_ADDER is
```

```
begin
```

```
    sum <= (not a and not b and cin) or
```

```
           (not a and b and not cin) or
```

```
           (a and not b and not cin) or
```

```
           (a and b and cin);
```

```
    cout <= (not a and b and cin) or
```

```
            (a and not b and cin) or
```

```
            (a and b and not cin) or
```

```
            (a and b and cin);
```

```
end BHV;
```

-----1-bit Adder Test File-----

LIBRARY IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

entity TEST\_ADD is

end TEST\_ADD;

-- Describes the functionality of the tesbench.

architecture TEST of TEST\_ADD is

    component BIT\_ADDER

        port( a, b, cin      : in  STD\_LOGIC;

            sum, cout      : out STD\_LOGIC );

    end component;

    for U1: BIT\_ADDER use entity WORK.BIT\_ADDER(BHV);

    signal A\_s, B\_s      : STD\_LOGIC;

    signal CIN\_s        : STD\_LOGIC;

    signal SUM\_s        : STD\_LOGIC;

    signal COUT\_s       : STD\_LOGIC;

begin

    U1: BIT\_ADDER port map (A\_s, B\_s, CIN\_s, SUM\_s, COUT\_s);

-- The process is where the actual testing is done.

process

begin

    -- Case 0 : 0+0 with carry in of 0.

-- Set the signals for the inputs.

A\_s <= '0';

B\_s <= '0';

CIN\_s <= '0';

wait for 10 ns;

assert ( SUM\_s = '0' ) report "Failed Case 0 - SUM" severity error;

assert ( COUT\_s = '0' ) report "Failed Case 0 - COUT" severity error;

wait for 40 ns;

-- Carry out the same process outlined above for the other 7 cases.

-- Case 1 : 0+0 with carry in of 1.

A\_s <= '0';

B\_s <= '0';

CIN\_s <= '1';

wait for 10 ns;

assert ( SUM\_s = '1' ) report "Failed Case 1 - SUM" severity error;

assert ( COUT\_s = '0' ) report "Failed Case 1 - COUT" severity error;

wait for 40 ns;

-- Case 2 : 0+1 with carry in of 0.

A\_s <= '0';

B\_s <= '1';

CIN\_s <= '0';

wait for 10 ns;

assert ( SUM\_s = '1' ) report "Failed Case 2 - SUM" severity error;

assert ( COUT\_s = '0' ) report "Failed Case 2 - COUT" severity error;

wait for 40 ns;

-- Case 3 : 0+1 with carry in of 1.

```
A_s <= '0';  
B_s <= '1';  
CIN_s <= '1';  
wait for 10 ns;  
assert ( SUM_s = '0' ) report "Failed Case 3 - SUM" severity error;  
assert ( COUT_s = '1' ) report "Failed Case 3 - COUT" severity error;  
wait for 40 ns;
```

-- Case 4 : 1+0 with carry in of 0.

```
A_s <= '1';  
B_s <= '0';  
CIN_s <= '0';  
wait for 10 ns;  
assert ( SUM_s = '1' ) report "Failed Case 4 - SUM" severity error;  
assert ( COUT_s = '0' ) report "Failed Case 4 - COUT" severity error;  
wait for 40 ns;
```

-- Case 5 : 1+0 with carry in of 1.

```
A_s <= '1';  
B_s <= '0';  
CIN_s <= '1';  
wait for 10 ns;  
assert ( SUM_s = '0' ) report "Failed Case 5 - SUM" severity error;  
assert ( COUT_s = '1' ) report "Failed Case 5 - COUT" severity error;  
wait for 40 ns;
```

-- Case 6 : 1+1 with carry in of 0.

```
A_s <= '1';  
B_s <= '1';  
CIN_s <= '0';
```

```

wait for 10 ns;

assert ( SUM_s = '0' ) report "Failed Case 6 - SUM" severity error;

assert ( COUT_s = '1' ) report "Failed Case 6 - COUT" severity error;

wait for 40 ns;

```

```

-- Case 7 : 1+1 with carry in of 1.

```

```

A_s <= '1';
B_s <= '1';
CIN_s <= '1';

wait for 10 ns;

assert ( SUM_s = '1' ) report "Failed Case 7 - SUM" severity error;

assert ( COUT_s = '1' ) report "Failed Case 7 - COUT" severity error;

wait for 40 ns;

```

```

end process;

```

```

END TEST;

```

```

-----2-bit Adder-----

```

```

LIBRARY IEEE;

```

```

use IEEE.STD_LOGIC_1164.ALL;

```

```

entity add2 is

```

```

    port( a, b          : in    STD_LOGIC_VECTOR(1 downto 0);
          cin           : in    STD_LOGIC;
          ans           : out   STD_LOGIC_VECTOR(1 downto 0);
          cout          : out   STD_LOGIC          );

```

```

end add2;

```

```

architecture STRUCTURE of add2 is

```

```

component BIT_ADDER
    port( a, b, cin      : in STD_LOGIC;
          sum, cout      : out STD_LOGIC );
end component;

signal c1 : STD_LOGIC;

begin

b_adder0: BIT_ADDER port map (a(0), b(0), cin, ans(0), c1);
b_adder1: BIT_ADDER port map (a(1), b(1), c1, ans(1), cout);
END STRUCTURE;

```

-----2-bit Adder Test File-----

```

LIBRARY IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

entity TEST_ADD2 is
end TEST_ADD2;

```

```

architecture TEST of TEST_ADD2 is

```

```

    component add2
        port( a, b          : in  STD_LOGIC_VECTOR(1 downto 0);
              cin : in  STD_LOGIC;
              ans         : out  STD_LOGIC_VECTOR(1 downto 0);
              cout        : out  STD_LOGIC          );
    end component;

```

```

    for U1: add2 use entity WORK.ADD2(STRUCTURE);

```

```
signal a, b          : STD_LOGIC_VECTOR(1 downto 0);  
signal cin  : STD_LOGIC;  
signal ans    : STD_LOGIC_VECTOR(1 downto 0);  
signal cout   : STD_LOGIC;
```

```
begin
```

```
U1: add2 port map (a,b,cin,ans,cout);
```

```
    process
```

```
    begin
```

```
        a <= "00";
```

```
        b <= "00";
```

```
        cin <= '0';
```

```
        wait for 10 ns;
```

```
        assert ( ans = "00" )      report "Failed Case 1 - ans" severity error;
```

```
        assert ( cout = '0' ) report "Failed Case 1 - cout" severity error;
```

```
        wait for 40 ns;
```

```
        a <= "00";
```

```
        b <= "00";
```

```
        cin <= '1';
```

```
        wait for 10 ns;
```

```
        assert ( ans = "01" )      report "Failed Case 2 - ans" severity error;
```

```
        assert ( cout = '0' ) report "Failed Case 2 - cout" severity error;
```

```
        wait for 40 ns;
```

```
        a <= "00";
```

```
b <= "01";  
cin <= '0';  
wait for 10 ns;  
assert ( ans = "01" )    report "Failed Case 3 - ans" severity error;  
assert ( cout = '0' ) report "Failed Case 3 - cout" severity error;  
wait for 40 ns;
```

```
a <= "00";  
b <= "01";  
cin <= '1';  
wait for 10 ns;  
assert ( ans = "10" )    report "Failed Case 4 - ans" severity error;  
assert ( cout = '0' ) report "Failed Case 4 - cout" severity error;  
wait for 40 ns;
```

```
a <= "00";  
b <= "10";  
cin <= '0';  
wait for 10 ns;  
assert ( ans = "10" )    report "Failed Case 5 - ans" severity error;  
assert ( cout = '0' ) report "Failed Case 5 - cout" severity error;  
wait for 40 ns;
```

```
a <= "00";  
b <= "10";  
cin <= '1';  
wait for 10 ns;  
assert ( ans = "11" )    report "Failed Case 6 - ans" severity error;
```



```
assert ( cout = '0' ) report "Failed Case 6 - cout" severity error;  
wait for 40 ns;
```

```
a <= "00";  
b <= "11";  
cin <= '1';  
wait for 10 ns;  
assert ( ans = "00" )    report "Failed Case 7 - ans" severity error;  
assert ( cout = '1' ) report "Failed Case 7 - cout" severity error;  
wait for 40 ns;
```

```
a <= "01";  
b <= "10";  
cin <= '0';  
wait for 10 ns;  
assert ( ans = "11" )    report "Failed Case 8 - ans" severity error;  
assert ( cout = '0' ) report "Failed Case 8 - cout" severity error;  
wait for 40 ns;
```

```
a <= "01";  
b <= "10";  
cin <= '1';  
wait for 10 ns;  
assert ( ans = "00" )    report "Failed Case 9 - ans" severity error;  
assert ( cout = '1' ) report "Failed Case 9 - cout" severity error;  
wait for 40 ns;
```

```

a <= "10";
b <= "10";
cin <= '1';
wait for 10 ns;
assert ( ans = "01" )    report "Failed Case 10 - ans" severity error;
assert ( cout = '1' ) report "Failed Case 10 - cout" severity error;
wait for 40 ns;

```

```

a <= "11";
b <= "11";
cin <= '1';
wait for 10 ns;
assert ( ans = "11" )    report "Failed Case 11 - ans" severity error;
assert ( cout = '1' ) report "Failed Case 11 - cout" severity error;
wait for 40 ns;

```

```

end process;

```

```

END TEST;

```

-----16-bit Adder Sub-----

```

LIBRARY IEEE;

```

```

use IEEE.STD_LOGIC_1164.ALL;

```

```

entity add16 is

```

```

    port( a, b          : in    STD_LOGIC_VECTOR(15 downto 0);
          cin : in STD_LOGIC;--_VECTOR(15 downto 0);
          ans      : out  STD_LOGIC_VECTOR(15 downto 0);

```

```

        overflow      : out   STD_LOGIC;
        cout          : out   STD_LOGIC      );
end add16;

```

architecture arch of add16 is

component add2

```

        port( a, b      : in     STD_LOGIC_VECTOR(1 downto 0);
              cin       : in     STD_LOGIC;
              ans        : out    STD_LOGIC_VECTOR(1 downto 0);
              cout       : out    STD_LOGIC      );
end component;

```

```

signal c1,c2,c3,c4,c5,c6,c7,c8 : STD_LOGIC;
signal mux : STD_LOGIC_VECTOR(15 downto 0);
begin

```

```

mux(0) <= cin xor b(0);
mux(1) <= cin xor b(1);
mux(2) <= cin xor b(2);
mux(3) <= cin xor b(3);
mux(4) <= cin xor b(4);
mux(5) <= cin xor b(5);
mux(6) <= cin xor b(6);
mux(7) <= cin xor b(7);
mux(8) <= cin xor b(8);
mux(9) <= cin xor b(9);
mux(10) <= cin xor b(10);
mux(11) <= cin xor b(11);
mux(12) <= cin xor b(12);

```

```

mux(13) <= cin xor b(13);
mux(14) <= cin xor b(14);
mux(15) <= cin xor b(15);

b_adder0: add2 port map (a(1 downto 0), mux(1 downto 0), cin, ans(1 downto 0), c1);
b_adder1: add2 port map (a(3 downto 2), mux(3 downto 2), c1, ans(3 downto 2), c2);
b_adder2: add2 port map (a(5 downto 4), mux(5 downto 4), c2, ans(5 downto 4), c3);
b_adder3: add2 port map (a(7 downto 6), mux(7 downto 6), c3, ans(7 downto 6), c4);
b_adder4: add2 port map (a(9 downto 8), mux(9 downto 8), c4, ans(9 downto 8), c5);
b_adder5: add2 port map (a(11 downto 10), mux(11 downto 10), c5, ans(11 downto 10), c6);
b_adder6: add2 port map (a(13 downto 12), mux(13 downto 12), c6, ans(13 downto 12), c7);
b_adder7: add2 port map (a(15 downto 14), mux(15 downto 14), c7, ans(15 downto 14), c8);

cout <= c8;

--overflow <= ((a(14)and (b(14) or c6)) or (c6 and b(14)))xor c7;
overflow <= c8 xor c7;

END arch;

```

-----16-bit Adder Sub Test File-----

```

LIBRARY IEEE;

```

```

use IEEE.STD_LOGIC_1164.ALL;

```

```

-- Declare a testbench. Notice that the testbench does not have any
-- input or output ports.

```

```

entity TEST_ADD16 is
end TEST_ADD16;

```

```

-- Describes the functionality of the tesbench.

```

architecture TEST of TEST\_ADD16 is

component add16

```
port( a, b          : in  STD_LOGIC_VECTOR(15 downto 0);
      cin : in  STD_LOGIC;--_VECTOR(15 downto 0);
      ans          : out      STD_LOGIC_VECTOR(15 downto 0);
      cout         : out  STD_LOGIC;
      overflow     : out  STD_LOGIC);
```

end component;

--for U1: add16 use entity WORK.add16(arch);

```
signal a, b          : STD_LOGIC_VECTOR(15 downto 0);
signal cin : STD_LOGIC;--_VECTOR(15 downto 0);
signal ans          : STD_LOGIC_VECTOR(15 downto 0);
signal cout         : STD_LOGIC;
signal overflow     : STD_LOGIC;
```

begin

U1: add16 port map (a,b,cin,ans,cout,overflow);

process

begin

-- pos + pos: no overflow

a <= "0001111111111111";

b <= "0000000000000001";

cin <= '0';

wait for 10 ns;

assert ( ans = "0010000000000000" )report "Failed Case 1 - ans" severity error;

assert ( cout = '0' ) report "Failed Case 1 - cout" severity error;

```

assert ( overflow = '0' ) report "Failed Case 1 - overflow" severity error;

wait for 40 ns;

-- pos + pos: overflow
a <= "0111111111111111";
b <= "0000000000000001";
cin <= '0';

wait for 10 ns;

assert ( ans = "1000000000000000" )report "Failed Case 2 - ans" severity error;
assert ( cout = '0' ) report "Failed Case 2 - cout" severity error;
assert ( overflow = '1' ) report "Failed Case 2 - overflow" severity error;
wait for 40 ns;


-- pos - pos: no overflow
a <= "0111111111111111";
b <= "0000000000000101";
cin <= '1';

wait for 10 ns;

assert ( ans = "011111111111010" )report "Failed Case 3 - ans" severity error;
assert ( cout = '1' ) report "Failed Case 3 - cout" severity error;
assert ( overflow = '0' ) report "Failed Case 3 - overflow" severity error;
wait for 40 ns;


-- neg + pos: no overflow
a <= "1111111111111111";
b <= "0000000000000001";
cin <= '0';

wait for 10 ns;

assert ( ans = "0000000000000000" )report "Failed Case 4 - ans" severity error;
assert ( cout = '1' ) report "Failed Case 4 - cout" severity error;
assert ( overflow = '0' ) report "Failed Case 4 - overflow" severity error;

```

```
wait for 40 ns;

-- neg + neg: no overflow
a <= "1111111111111111";
b <= "1111111111111111";
cin <= '0';
wait for 10 ns;
assert ( ans = "111111111111110" )report "Failed Case 5 - ans" severity error;
assert ( cout = '1' ) report "Failed Case 5 - cout" severity error;
assert ( overflow = '0' ) report "Failed Case 5 - overflow" severity error;
wait for 40 ns;

-- neg - pos: overflow
a <= "1000000000000000";
b <= "0000000000000001";
cin <= '1';
wait for 10 ns;
assert ( ans = "011111111111111" )report "Failed Case 6 - ans" severity error;
assert ( cout = '1' ) report "Failed Case 6 - cout" severity error;
assert ( overflow = '1' ) report "Failed Case 6 - overflow" severity error;
wait for 40 ns;
end process;
END TEST;
```